

## In-Class Exercise: High Pass Filter.

NAME:

February 7, 2018

Figure 1 shows the schematic of a high-pass filter. As you can see the resistor and capacitor are reversed compared to the low pass filter.

1. Derive the transfer function of this circuit  $G(j\omega)$  using the voltage divider rule and the impedance of a capacitor.
2. Fill out this table:

	$G(j\omega)$	$ G(j\omega) _{dB}$	$\phi$ (Phase)
$\omega\tau \ll 1$			
$\omega\tau = 1$			
$\omega\tau \gg 1$			

3. Draw the Bode plot of this transfer function on the back of this page.

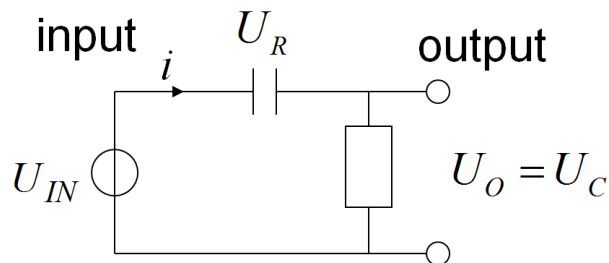


Figure 1: High pass passive filter consisting of a resistor and a capacitor, the output voltage is across the resistor.